



17333

21415

3 Hours/100 Marks

Seat No.

--	--	--	--	--	--	--	--	--	--

-
- Instructions:** (1) **All** questions are **compulsory**.
(2) Figures to the **right** indicate **full** marks.
(3) *Mobile Phone, Pager and any other Electronic Communication devices are **not permissible** in Examination Hall.*
-

MARKS

1. a) Attempt **any six** :

12

- i) What is positive logic and negative logic in digital system ?
- ii) Define fan in and noise margin.
- iii) Draw symbol and truth table of 3 i/p OR gate.
- iv) State DeMorgan's theorem.
- v) Convert the following :
 - a) $(156)_{10} \rightarrow (?)_{BCD}$ and $(?)_2$
- vi) List any four Boolean laws.
- vii) Define encoder. Write the number of IC used as decimal to BCD encoder.
- viii) Define any two specifications of ADC.

b) Attempt **any two** :

8

- i) Compare TTL and CMOS logic family on the basis of propagation delay, power dissipation, fan out and components used.
- ii) Design OR and AND gate using NOR gate only.
- iii) Perform the following binary subtraction using 2's complement :
 - 1) $(54)_{10} - (33)_{10} = ?$
 - 2) $(48)_{10} - (68)_{10} = ?$

P.T.O.



2. Attempt any 4 :

16

- a) Draw X-OR gate using NAND gate only. Also write O/P of each gate.
- b) Simplify the following equation using boolean laws and realize it using basic gates only. $Y = ABC + A\bar{B}C + \bar{A}BC + \bar{A}\bar{B}C$.
- c) Perform the following BCD arithmetic :
- 1) $(630)_{10} + (468)_{10}$
 - 2) $(245)_{10} + (186)_{10}$.
- d) Simplify the following equation using k-map and realize it using logic gates.
 $Y = \sum m(0, 1, 2, 3, 8, 10) + \sum d(5, 7)$.
- e) Design Half adder using k-map and basic gates.
- f) Draw block diagram of decimal to BCD encoder and write its truth table.

3. Attempt any four :

16

- a) Simplify using DeMorgans theorem and realize it using basic gates.
 $Y = \overline{(AB + \bar{A}\bar{B})}(\overline{AB + \bar{A}\bar{B}})$.
- b) Design 8 : 1, MUX using 2 : 1 MUX and 4 : 1 MUX.
- c) Minimize the following equation using k-map.
- 1) $Y = \sum m(0, 1, 2, 4, 5, 6)$
 - 2) $Y = \prod m(0, 2, 4, 5)$.
- d) Design 1 : 8 demux using basic gates.
- e) Explain different triggering methods used in f.f.
- f) Explain working of PIPO with neat logic diagram and timing diagram.



4. Attempt **any four** :

16

- a) Explain working of 2 bit asynchronous counter with the help of neat diagram, truth table and timing diagram.
- b) Explain successive approximation type ADC with neat diagram.
- c) Describe working of RS ff using NAND gates only.
- d) What is race around condition ? How to eliminate it ?
- e) Define memory. Give classification of memory. Compare PROM and EPROM (any 2 pts.).
- f) What is the need of data converters ? List specifications of DAC.

5. Attempt **any four** :

16

- a) Convert the following :
 - 1) $(366.54)_8 \rightarrow (?)_{10}$ and
 - 2) $(2015.32)_{10} \rightarrow (?)_{16}$.
- b) Compare combinational logic circuit and sequential logic circuit (any 4 pts.)
- c) Simplify the following and realize it.
 $Y = A + \bar{A} \bar{B} C + \bar{A} \bar{B} \bar{C} + ABC + \bar{A} \bar{B}$.
- d) Explain working of 3 bit synchronous counter with the help of neat logic diagram, timing diagram and truth table.
- e) Describe block diagram of digital comparator and write truth table of 2 bit comparator.
- f) Compare synchronous and asynchronous counter. (any 4 pts.)

6. Attempt **any two** :

16

- a) i) Convert the following SOP equation into standard SOP equation. 2
 $Y = AB + \bar{A} B + A \bar{B} \bar{C}$.
- ii) List any four applications of multiplexer and implement the following logic expression using 16:1 MUX. 6
 $Y = \sum m(0, 3, 5, 6, 7, 10, 13)$.

**MARKS**

- b) i) Draw symbol and truth table of negative edge triggered D.FF and positive edge triggered JK FF. **2**
- ii) What is modulus of counter ? Show the method to determine the no. of flip flops for a mod-52 counter. **4**
- iii) Draw only logic diagram of SIPO. **2**
- c) i) A DAC has a full scale analog O/P of 10V and accepts 4 binary bits as i/ps. Find the voltage corresponding to each analog step. **4**
- ii) Describe working of R-2R Ladder type DAC. **4**
-